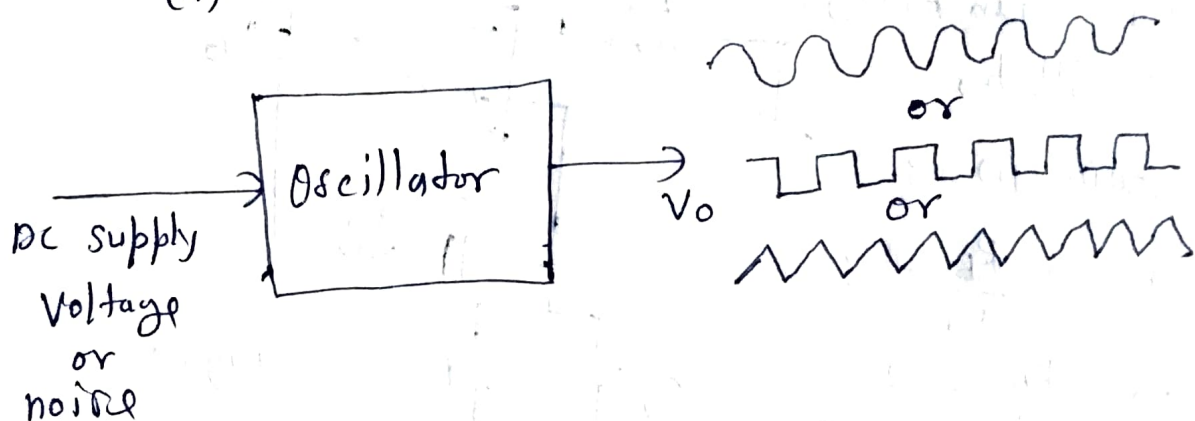


# Oscillator

⇒ An oscillator is a circuit that produces a periodically oscillating waveform on its output with dc input. The output voltage can be either sinusoidal or nonsinusoidal, depending on the type of oscillator.

⇒ Basic classifications for oscillators are


- (i) feedback oscillator
- (ii) Relaxation oscillator.



(\*) Conditions of Oscillation!

there are two conditions for oscillation.

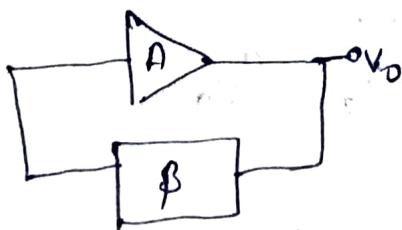- (i) the phase shift around the feedback loop must be  $0^\circ$  ( $2\pi n$ )
- (ii) loop gain must be '1' i.e.  $AB = 1$



phase shift = 1

loop gain  $AB = 1$

## ⊗ Types of sinusoidal oscillators:

- (i) Wien bridge oscillator.
- (ii) RC phase-shift oscillator.
- (iii) LC oscillator.
- (iv) crystal oscillator.

### (i) Wien bridge oscillator:-

For Wien bridge oscillator

$$\text{gain } (A) = 3$$

$$\text{or } 1 + \frac{R_B}{R_A} = 3$$

$$\Rightarrow \frac{R_B}{R_A} = 2$$

$$\Rightarrow \boxed{R_B = 2R_A}$$

↑ condition of oscillation.

We know that

$$A \cdot \beta = 1$$

$$\Rightarrow 3 \cdot \beta = 1 \Rightarrow$$

$$\boxed{\beta = \frac{1}{3}}$$

$\Rightarrow$  For Fig (1) the feedback network can be written as shown as.

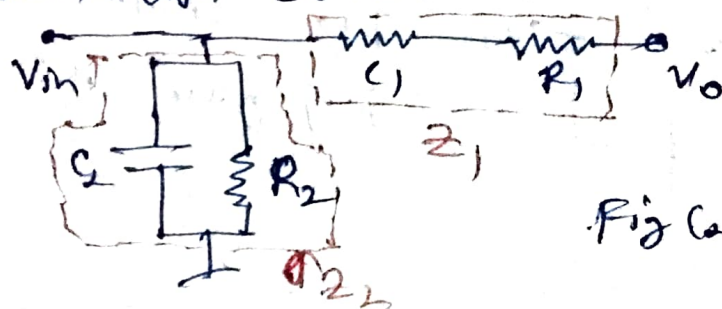


Fig (a)

from Fig (2)

$$\frac{V_o}{V_{in}} = \frac{Z_2}{Z_1 + Z_2} \quad \text{--- (A)}$$

$$\text{Since } Z_1 = R_1 + \frac{1}{sC_1}$$

$$Z_2 = R_2 \parallel \frac{1}{sC_2}$$

$$\Rightarrow \frac{V_o}{V_{in}} = \frac{R_2 \parallel \frac{1}{sC_2}}{R_1 + \frac{1}{sC_1} + \left\{ R_2 \parallel \frac{1}{sC_2} \right\}}$$

$$\Rightarrow \frac{V_o}{V_{in}} = \frac{R_2 \times \frac{1}{sC_2}}{R_2 + \frac{1}{sC_2}}$$

$$\frac{R_1 + \frac{1}{sC_1} + \frac{R_2 \times \frac{1}{sC_2}}{R_2 + \frac{1}{sC_2}}}{R_2 \parallel \frac{1}{sC_2}}$$

$$\Rightarrow \frac{V_o}{V_{in}} = \frac{R_1 R_2 + \frac{R_1}{sC_2} + \frac{R_2}{sC_1} + \frac{1}{s^2 C_1 C_2} + \frac{R_2}{sC_2}}{s R_2 C_1}$$

$$\Rightarrow \frac{V_o}{V_{in}} = \frac{1 + s^2 R_1 R_2 C_1 C_2 + s [R_1 C_1 + R_2 C_2 + R_2 C_1]}{s R_2 C_1}$$

$$\text{put } s = j\omega$$

$$\Rightarrow \frac{V_o}{V_{in}} = \frac{j\omega R_2 C_1}{1 - \omega^2 R_1 R_2 C_1 C_2 + j\omega [R_1 C_1 + R_2 C_2 + R_2 C_1]} \quad \text{--- (B)}$$

for oscillation

$$\text{phase shift } \left( \frac{V_o}{V_{in}} \right) = 0$$

$$\Rightarrow 1 - \omega^2 R_1 R_2 C_1 C_2 = 0$$

$$\Rightarrow \omega^2 = \frac{1}{R_1 R_2 C_1 C_2}$$

$$\Rightarrow \omega = \sqrt{\frac{1}{R_1 R_2 C_1 C_2}}$$

$$\Rightarrow \boxed{f = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}}$$

at this frequency eqn. (1) becomes -

$$\frac{V_o}{V_{in}} = \frac{R_2 C_1}{R_1 C_1 + R_2 C_2 + R_2 C_1}$$

$$\Rightarrow \beta = \frac{R_2 C_1}{R_1 C_1 + R_2 C_2 + R_2 C_1}$$

Since  $A \cdot \beta = 1$

$$\Rightarrow A = \frac{1}{\beta}$$

$$\Rightarrow A = \frac{R_1 C_1 + R_2 C_2 + R_2 C_1}{R_2 C_1}$$

$$\Rightarrow A = \frac{R_1}{R_2} + \frac{C_2}{C_1} + 1$$


$$\Rightarrow 1 + \frac{R_b}{R_a} = \frac{R_1}{R_2} + \frac{C_2}{C_1} + 1$$

$$\Rightarrow \boxed{\frac{R_b}{R_a} = \frac{R_1}{R_2} + \frac{C_2}{C_1}}$$

Condition for oscillation


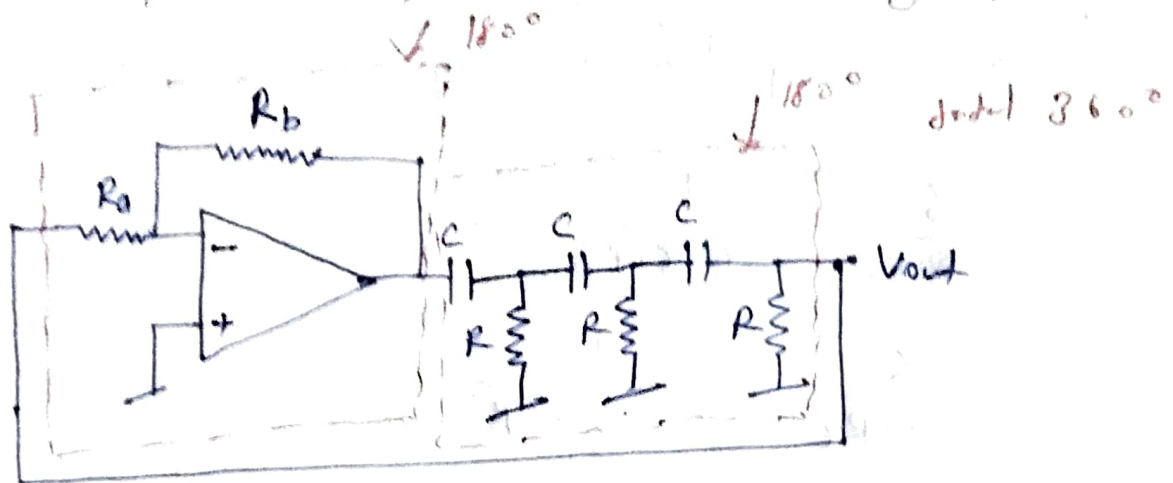
# ⊗ RC-phase shift Oscillator using op-amp:



Fig(1)


for oscillation total phase shift =  $0^\circ$  or  $360^\circ$

for RC-phase shift oscillator

$$A = 29 \quad \& \quad \beta = \frac{1}{29}$$

$$= \boxed{A \cdot \beta = 1}$$

the feedback network is given as:

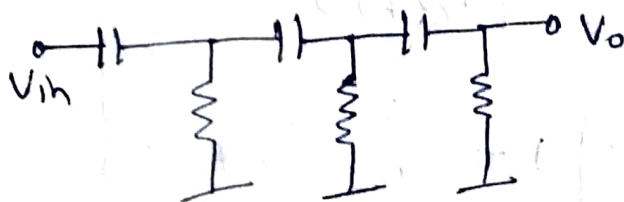

Fig(2)

From Fig (2)

$$V_{in} = V_o \left[ 1 + \frac{6}{sRC} + \frac{5}{s^2 R^2 C^2} + \frac{1}{s^3 R^3 C^3} \right]$$

$$\Rightarrow \frac{V_{in}}{V_o} = 1 + \frac{6}{sRC} + \frac{5}{s^2 R^2 C^2} + \frac{1}{s^3 R^3 C^3}$$

$$\Rightarrow \frac{V_{in}}{V_o} = 1 + \frac{6}{j\omega RC} - \frac{5}{\omega^2 R^2 C^2} - \frac{1}{j\omega^3 R^3 C^3} \quad \text{--- (A)}$$

for oscillation frequency imaginary part of above equation is equal to zero

$$\Rightarrow \frac{6}{\omega RC} - \frac{1}{\omega^3 C^3 R^3} = 0$$

$$\Rightarrow \frac{6}{\omega RC} = \frac{1}{\omega^3 C^3 R^3}$$

$$\Rightarrow \omega^2 = \frac{1}{R^2 C^2 6}$$

$$\Rightarrow \omega = \frac{1}{RC\sqrt{6}}$$

$$\Rightarrow \boxed{f = \frac{1}{2\pi RC\sqrt{6}}}$$

at resonant frequency eqn. (A) becomes.

$$V_{in} = V_o \left[ 1 - \frac{5}{\omega^2 C^2 R^2} \right]$$

$$\Rightarrow \text{or } V_{in} = V_o \left[ 1 - \frac{5}{\frac{1}{R^2 C^2 6} \times R^2 C^2} \right]$$

$$\Rightarrow V_{in} = V_o [1 - 30]$$

$$\Rightarrow V_{in} = -29 V_o$$

$$\Rightarrow \frac{V_o}{V_{in}} = -29$$

$$\Rightarrow \left| \frac{V_o}{V_{in}} \right| = 29 \Rightarrow \angle \left[ \frac{V_o}{V_{in}} \right] = -180^\circ$$